

minimum Range of R

3. Over the entire range of D that you calculated in the last part, if you now wish to operate the converter in CCM, what should be the value of L that you will use? What is the corresponding variation in V ? (4+1+1)

@ $D = D_{\min}$, $K_{crit} = 0.639^2 = 0.4083$
 for $R = 300 \Omega$.
 minimum L : DCM-CCM boundary at R_{\max}

$$\frac{2L}{R_{\max} T} = 0.4083$$

$$L = \frac{0.4083 \times 300 \times 20}{2} \mu H$$

$$= 1.224 \text{ mH}$$

$$V @ D = 0.361 \Rightarrow \left(\frac{0.361}{1-0.361} \right) \times 12$$

$$= 6.78 \text{ V}$$

Ans: $L = 1.224 \text{ mH}$, $V_{\min} = 6.78 \text{ V}$, $V_{\max} = 15 \text{ V}$

3